



$$V_{CC} = R_C(I_C + I_B) + R_B I_B + V_{BE} \quad \text{--- (1)}$$

直流電流増幅率の定義式 $h_{FE} = \frac{I_C}{I_B} \Rightarrow \underline{I_B = \frac{I_C}{h_{FE}}}$

(1) 式に代入

$$V_{CC} = R_C I_C + \frac{R_C I_C}{h_{FE}} + R_B \frac{I_C}{h_{FE}} + V_{BE}$$

$$= R_C I_C \left(1 + \frac{1}{h_{FE}}\right) + R_B \frac{I_C}{h_{FE}} + V_{BE} \quad \rightarrow \text{式変形をして } R_B = ? \text{ の形にする。}$$

$$R_B \frac{I_C}{h_{FE}} = V_{CC} - R_C I_C \left(1 + \frac{1}{h_{FE}}\right) - V_{BE}$$

$$R_B = \frac{V_{CC} h_{FE}}{I_C} - R_C h_{FE} - R_C - \frac{V_{BE} h_{FE}}{I_C} = -R_C (h_{FE} + 1) + \frac{V_{CC} h_{FE} - V_{BE} h_{FE}}{I_C}$$

$$R_B = -R_C (h_{FE} + 1) + \frac{h_{FE}}{I_C} (V_{CC} - V_{BE})$$

$$\therefore R_B = \frac{h_{FE}}{I_C} (V_{CC} - V_{BE}) - R_C (h_{FE} + 1)$$

数値を代入

$$R_B = \frac{100}{2 \text{ mA}} (12 - 0.64) - 3 \text{ k}\Omega (100 + 1)$$

$$= \frac{100}{2 \times 10^{-3}} \times 11.36 - 3000 \times 101$$

$$= \frac{100 \times 11.36}{0.002} - 303000 = 265000 = 265 \times 10^3$$

$$= \underline{265 \text{ [k}\Omega\text{]}} \quad \text{(総)}$$

pyllt11